

Date:16-09-2022

Assignment-6

Question 1: Write a Verilog code to design a 4:1 Multiplexer and verify the same.

Code:

Testbench Code:

```
//21BCP322
//Akshat shah
module tb_MUX;

    reg S0,S1,I0,I1,I2,I3;
    wire Y;

    MUX M4x1(S0,S1,I0,I1,I2,I3,Y);

    initi
    al
    be
    gin
        S0=0; S1=0; I0=0 ;I1=0;I2=0;I3=1; #1
        $display("S0=%b S1=%b",S0,S1);
        $display("Y=%b",Y);

        S0=0; S1=1; I0=1 ;I1=0;I2=1;I3=1; #1
        $display("S0=%b S1=%b",S0,S1);
        $display("Y=%b",Y);

        S0=1; S1=0; I0=0 ;I1=0;I2=1;I3=0; #1
        $display("S0=%b S1=%b",S0,S1);
        $display("Y=%b",Y);

        S0=1; S1=1; I0=0 ;I1=1;I2=0;I3=1; #1
        $display("S0=%b S1=%b",S0,S1);
        $display("Y=%b",Y);
    end
    init
    ial
    beg
    in
        $dumpfile("dump.vcd");
        $dumpvars(
        1); end
endmodule
```

Design Code:

```
//21BCP322
module MUX(input s0,s1,I0,I1,I2,I3, output y);
    wire s0_not,s1_not,a,b,c,d;
    not(s0_not,s0);
    not(s1_not,s1);
    assign a = s0 & s1 & I0;
    assign b = s0_not & s1 &
    I1; assign c = s0 & s1_not
    & I2;
    assign d = s0_not & s1_not & I3;
    assign y = a | b | c | d;
endmodule
```

Output:

```
[2022-10-04 13:03:45 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
S0=0 S1=0
Y=1
S0=0 S1=1
Y=0
S0=1 S1=0
Y=1
S0=1 S1=1
Y=0
Finding VCD file...
./dump.vcd
[2022-10-04 13:03:45 EDT] Opening EPWave...
Done
```

Figure 1: Output of 4:1 Multiplexer

Waveform:


 


Figure 2: Waveform of 4:1 Multiplexer

Circuit diagram:

 

Question 2: Write a Verilog code to design an 8:1 Multiplexer and verify the same.

Testbench Code:

```
//21BCP322
//Akshat shah
module tb_MUX;

    reg S0,S1,S2;
    reg I0,I1,I2,I3,I4,I5,I6,I7;
    wire Y;

    MUX M8x1(S0,S1,S2,I0,I1,I2,I3,I4,I5,I6,I7,Y);

    initial
        begin

            S0=0;S1=0;S2=0;I0=0;I1=0;I2=0;I3=0;I4=0;I5=0;I6=0;I7=1; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);
            S0=0;S1=0;S2=1;I0=1;I1=0;I2=0;I3=0;I4=0;I5=0;I6=1;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);

            S0=0;S1=1;S2=0;I0=0;I1=0;I2=0;I3=0;I4=0;I5=1;I6=0;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);

            S0=0;S1=1;S2=1;I0=0;I1=0;I2=0;I3=0;I4=1;I5=0;I6=0;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);

            S0=1;S1=0;S2=0;I0=0;I1=0;I2=0;I3=1;I4=0;I5=0;I6=0;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);

            S0=1;S1=0;S2=1;I0=0;I1=0;I2=1;I3=0;I4=0;I5=0;I6=0;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);

            S0=1;S1=1;S2=0;I0=0;I1=1;I2=0;I3=0;I4=0;I5=0;I6=0;I7=0; #1
                $display("S0=%b S1=%b S2=%b",S0,S1,S2);
                $display("Y=%b",Y);
```

Design Code:

```
//21BCP291
Module
MUX(s0,s1,s2,A0,A1,A2,A3,A4,A5,A6,A7,y);
    input s0,s1,s2;
    input A0,A1,A2,A3,A4,A5,A6,A7;
    output y;
    wire s0_not,s1_not,s2_not;
    wire B0,B1,B2,B3,B4,B5,B6;
    not(s0_not,s0);
    not(s1_not,s1);
    not(s2_not,s2);
    assign B0 = s0 & s1 & s2 & A0;
    assign B1 = s0 & s1 & s2_not & A1;
    assign B2 = s0 & s1_not & s2 & A2;
    assign B3 = s0 & s1_not & s2_not & A3;
    assign B4 = s0_not & s1 & s2 & A4;
    assign B5 = s0_not & s1 & s2_not & A5;
    Assign B6= s0_not & s1_not & s2 & A6;
    Assign B7=s0_not & s1_not & s2 & A7;

    Assign y=B0|B1|B2|B3|B4|B5|B6|B7;

endmodule
```


```
S0=1;S1=1;S2=1;I0=1;I1=0;I2=0;I3=0;I4=0;I5=0;I6=0;I7=0;#1
```

```
$display("S0=%b S1=%b S2=%b",S0,S1,S2);  
$display("Y=%b",Y);
```

```
end  
initial  
begin  
$dumpfile("dump.vcd");  
$dumpvars(1);  
end  
endmodule
```

Table 2:Code of 8:1 Multiplexer

Circuit diagram(8:1 MUX):

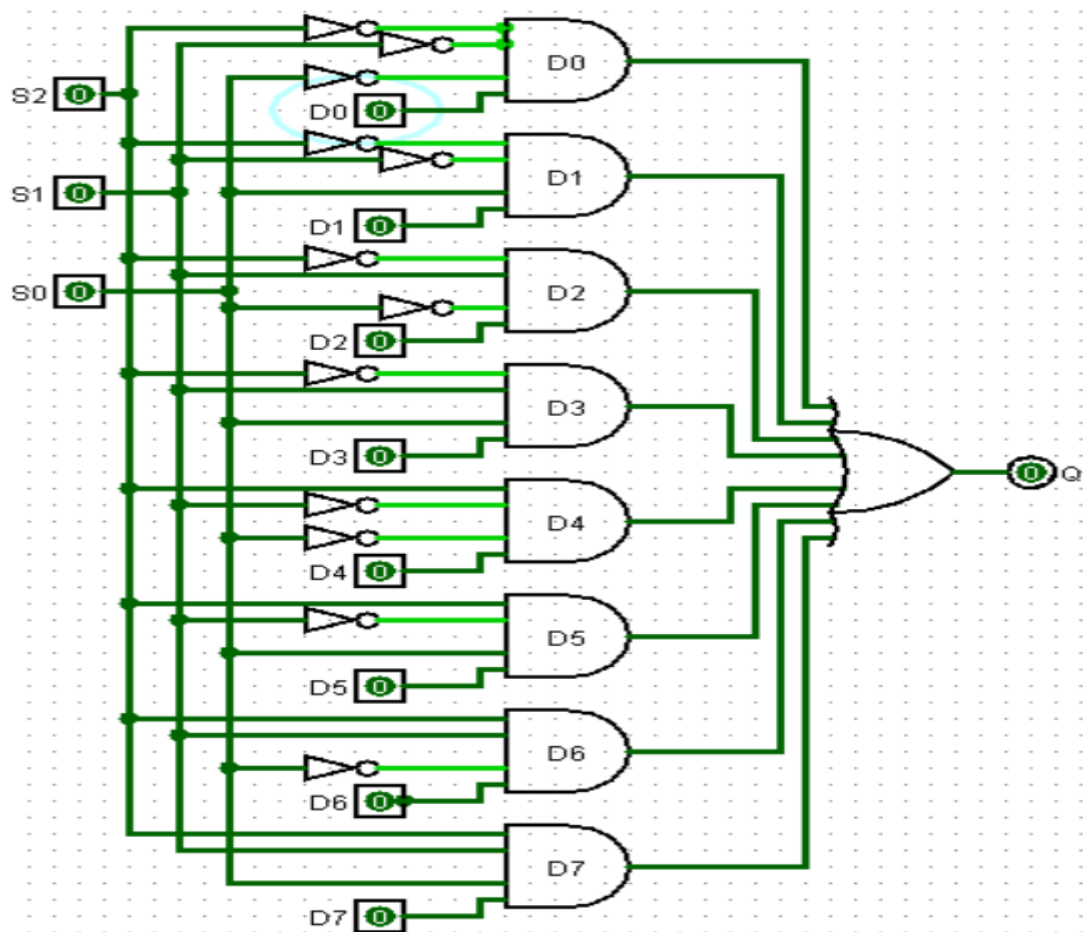


Output:

```
[2022-10-04 13:10:37 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
design.sv:18: warning: implicit definition of wire logic TestModule.M4x1.B7.
VCD info: dumpfile dump.vcd opened for output.
S0=0 S1=0 S2=0
Y=1
S0=0 S1=0 S2=1
Y=1
S0=0 S1=1 S2=0
Y=1
S0=0 S1=1 S2=1
Y=1
S0=1 S1=0 S2=0
Y=1
S0=1 S1=0 S2=1
Y=1
S0=1 S1=1 S2=0
Y=1
S0=1 S1=1 S2=1
Y=1
Finding VCD file...
./dump.vcd
[2022-10-04 13:10:38 EDT] Opening EPWave...
Done
```

Figure 3: Output of 8:1 Multiplexer

Waveform:

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Figure 4: Waveform of 8:1 Multiplexer

Question 3: Write a Verilog code to design a 1:4 Demultiplexer and verify the same.

Testbench Code:

```
//21BCP322
//Akshat Shah
module
tb_DEMUX;

    reg S0,S1,E;
    wire O0,O1,O2,O3;

    DEMUX DM4x1(S0,S1,E,O0,O1,O2,O3);

    initial
    begin
        S0=0; S1=0; E=0; #1
        $display("S0=%b S1=%b E=%b",S0,S1,E);

        $display("O0=%b O1=%b O2=%b
O3=%b",O0,O1,O2,O3);

        S0=0; S1=0; E=1;#1
        $display("S0=%b S1=%b E=%b",S0,S1,E);
        $display("O0=%b O1=%b O2=%b
O3=%b",O0,O1,O2,O3);

        S0=0; S1=1; E=1;#1
        $display("S0=%b S1=%b E=%b",S0,S1,E);
        $display("O0=%b O1=%b O2=%b
O3=%b",O0,O1,O2,O3);

        S0=1; S1=0; E=1;#1
        $display("S0=%b S1=%b E=%b",S0,S1,E);
        $display("O0=%b O1=%b O2=%b
O3=%b",O0,O1,O2,O3);

        S0=1; S1=1; E=1;#1
        $display("S0=%b S1=%b E=%b",S0,S1,E);
        $display("O0=%b O1=%b O2=%b
O3=%b",O0,O1,O2,O3);
    end
    initial
    begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
    end
endmodule
```

Design Code:

```
//21BCP322
module DEMUX(input s0,s1,E, output
o0,o1,o2,o3);
    wire s0_not,s1_not,x,y,z,w;
    not(s0_not,s0);
    not(s1_not,s1);
    assign o0 = s0 & s1 & E;
    assign o1 = s0_not & s1 & E;
    assign o2 = s0 & s1_not & E;
    assign o3 = s0_not & s1_not & E;

endmodule
```

Output:

```
[2022-10-04 13:13:34 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
```

```
VCD info: dumpfile dump.vcd opened for output.
```

```
S0=0 S1=0 E=0
```

```
00=0 01=0 02=0 03=0
```

```
S0=0 S1=0 E=1
```

```
00=0 01=0 02=0 03=1
```

```
S0=0 S1=1 E=1
```

```
00=0 01=1 02=0 03=0
```

```
S0=1 S1=0 E=1
```

```
00=0 01=0 02=1 03=0
```

```
S0=1 S1=1 E=1
```

```
00=1 01=0 02=0 03=0
```

```
Finding VCD file...
```

```
./dump.vcd
```

```
[2022-10-04 13:13:34 EDT] Opening EPWave...
```

```
Done
```

Figure 5: Output of 1:4 Demultiplexer

Waveform:



 


Figure 6: Waveform of 1:4 Demultiplexer

 

Circuit diagram of 1:4 demultiplexer

 

Question 4: Write a Verilog code to design a 1:8 Demultiplexer and verify the same.

Testbench code:

```
//21BCP322
//Akshat shah
module
tb_DEMUX;

    reg S0,S1,S2,E;
    wire O0,O1,O2,O3,O4,O5,O6,O7;

    DEMUX
DM8x1(S0,S1,S2,E,O0,O1,O2,O3,O4,O5,O6,O
7);

    initial
    begin
        S0=0; S1=0; S2=0; E=0; #1
        $display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
        $display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

        S0=0; S1=0; S2=0; E=1; #1
        $display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
        $display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

        S0=0; S1=1; S2=1; E=1; #1
        $display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
        $display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

        S0=0; S1=1; S2=0; E=1; #1
        $display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);

        $display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);
```

Design code:

```
//21BCP322
module
DEMUX(s0,s1,s2,E,A0,A1,A2,A3,A4,A5,A6,A
7);
    input s0,s1,s2,E;
    output A0,A1,A2,A3,A4,A5,A6,A7;
    wire s0_not,s1_not,s2_not;
    not(s0_not,s0);
    not(s1_not,s1);
    not(s2_not,s2);
    assign A0 = s0 & s1 & s2 & E;
    assign A1 = s0 & s1 & s2_not & E;
    assign A2 = s0 & s1_not & s2 & E;
    assign A3 = s0 & s1_not & s2_not & E;
    assign A4 = s0_not & s1 & s2 & E;
    assign A5 = s0_not & s1 & s2_not & E;
    assign A6 = s0_not & s1_not & s2 & E;
    assign A7 = s0_not & s1_not & s2_not & E;

endmodule
```

```

$display("S0 S0=0; S1=0; S2=1; E=1; #1
      =%b S1=%b S2=0 E=%b",S0,S1,S2,E);
$display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

      S0=1; S1=0; S2=0; E=1; #1
$display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
$display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

      S0=1; S1=0; S2=1; E=1; #1
$display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
$display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

      S0=1; S1=1; S2=0; E=1; #1
$display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
$display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

      S0=1; S1=1; S2=1; E=1; #1
$display("S0=%b S1=%b S2=0
E=%b",S0,S1,S2,E);
$display("O0=%b O1=%b O2=%b O3=%b
O4=%b O5=%b O6=&b
O7=%b",O0,O1,O2,O3,O4,O5,O6,O7);

end
initial
begin
$dumpfile("dump.vcd");
$dumppvars(1);
end
endmodule

```

Output:

```

[2022-10-04 13:16:19 EDT] Iverilog "-wall" design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
S0=0 S1=0 S2=0 E=00
O0=0 O1=0 O2=0 O3=0 O4=0 O5=0 O6=&b O7=00
S0=0 S1=0 S2=0 E=01
O0=0 O1=0 O2=0 O3=0 O4=0 O5=0 O6=&b O7=01
S0=0 S1=1 S2=0 E=11
O0=0 O1=0 O2=0 O3=0 O4=1 O5=0 O6=&b O7=00
S0=0 S1=1 S2=0 E=01
O0=0 O1=0 O2=0 O3=0 O4=0 O5=1 O6=&b O7=00
S0=0 S1=0 S2=0 E=11
O0=0 O1=0 O2=0 O3=0 O4=0 O5=0 O6=&b O7=10
S0=1 S1=0 S2=0 E=01
O0=0 O1=0 O2=0 O3=1 O4=0 O5=0 O6=&b O7=00
S0=1 S1=0 S2=0 E=11
O0=0 O1=0 O2=1 O3=0 O4=0 O5=0 O6=&b O7=00
S0=1 S1=1 S2=0 E=01
O0=0 O1=1 O2=0 O3=0 O4=0 O5=0 O6=&b O7=00
S0=1 S1=1 S2=0 E=11
O0=1 O1=0 O2=0 O3=0 O4=0 O5=0 O6=&b O7=00
Finding VCD file...
./dump.vcd
[2022-10-04 13:16:19 EDT] Opening EPWave...
Done

```

Waveform:


 


Figure 8: Waveform of 1:8 Demultiplexer

Circuit diagram:

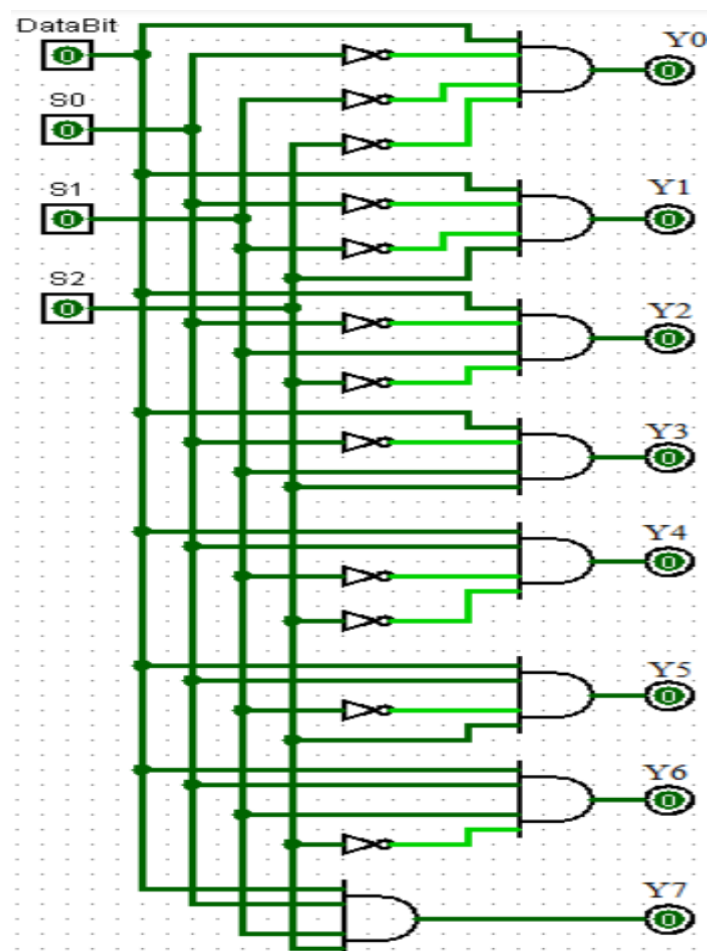

Question 5: Write a Verilog code to design a 3:8 Decoder and verify the same.

Code:

Testbench:

```
//21BCP322
// Akshat shah
module tb_Dec;

    reg I0,I1,I2;
    wire Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7;

    Decoder
    D1(I0,I1,I2,Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);
    initial
    begin
        I0=0;I1=0;I2=0; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
        $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

        I0=0;I1=0;I2=1; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
        $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

        I0=0;I1=1;I2=0; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
        $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

        I0=0;I1=1;I2=1; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
        $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

        I0=1;I1=0;I2=0; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
        $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

        I0=1;I1=0;I2=1; #1
        $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
```

Design:

```
//21BCP322
module
Decoder(B0,B1,B2,A0,A1,A2,A3,A4,A5,A6,A7);
    input B0,B1,B2;
    output A0,A1,A2,A3,A4,A5,A6,A7;
    assign A0 = ~B0 & ~B1 & ~B2;
    assign A1 = ~B0 & ~B1 & B2;
    assign A2 = ~B0 & B1 & ~B2;
    assign A3 = ~B0 & B1 & B2;
    assign A4 = B0 & ~B1 & ~B2;
    assign A5 = B0 & ~B1 & B2;
    assign A6 = B0 & B1 & ~B2;
    assign A7 = B0 & B1 & B2;

endmodule
```

```

    $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

    I0=1;I1=1;I2=0; #1
    $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
    $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

    I0=1;I1=1;I2=1; #1
    $display("I0=%b I1=%b
I2=%b",I0,I1,I2);
    $display("Y0=%b Y1=%b Y2=%b Y3=%b
Y4=%b Y5=%b Y6=%b
Y7=%b",Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);

end
initial
begin
$dumpfile("dump.vcd");
$dumpvars(1);
end
endmodule

```

Output:

```

[2022-10-04 13:40:51 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
I0=0 I1=0 I2=0
Y0=1 Y1=0 Y2=0 Y3=0 Y4=0 Y5=0 Y6=0 Y7=0
I0=0 I1=0 I2=1
Y0=0 Y1=1 Y2=0 Y3=0 Y4=0 Y5=0 Y6=0 Y7=0
I0=0 I1=1 I2=0
Y0=0 Y1=0 Y2=1 Y3=0 Y4=0 Y5=0 Y6=0 Y7=0
I0=0 I1=1 I2=1
Y0=0 Y1=0 Y2=0 Y3=1 Y4=0 Y5=0 Y6=0 Y7=0
I0=1 I1=0 I2=0
Y0=0 Y1=0 Y2=0 Y3=0 Y4=1 Y5=0 Y6=0 Y7=0
I0=1 I1=0 I2=1
Y0=0 Y1=0 Y2=0 Y3=0 Y4=0 Y5=1 Y6=0 Y7=0
I0=1 I1=1 I2=0
Y0=0 Y1=0 Y2=0 Y3=0 Y4=0 Y5=0 Y6=1 Y7=0
I0=1 I1=1 I2=1
Y0=0 Y1=0 Y2=0 Y3=0 Y4=0 Y5=0 Y6=0 Y7=1
Finding VCD file...
./dump.vcd
[2022-10-04 13:40:52 EDT] Opening EPWave...
Done

```

Figure 9: Output of 3:8 Decoder

Waveform:


 


Figure 10: Waveform of 3:8 Decoder

Circuit diagram:

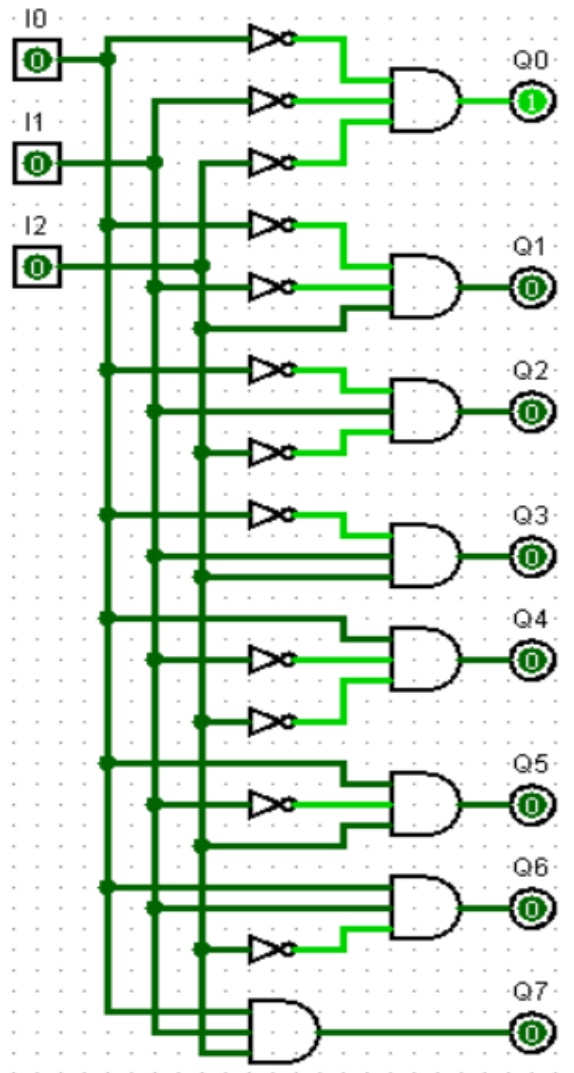

Question 6: Write a Verilog code to design a 8:3 Encoder and verify the same.

Testbench:

```
//21BCP322
//Akshat shah
module tb_Enc;

    reg I0,I1,I2,I3,I4,I5,I6,I7;
    wire Y0,Y1,Y2;

    Encoder
    E1(I0,I1,I2,I3,I4,I5,I6,I7,Y0,Y1,Y2);
    initial
    begin

        I0=1;I1=0;I2=0;I3=0;I4=0;I5=0;I6=0;I7=0; #1
        $display("I0=%b I1=%b I2=%b I3=%b
        I4=%b I5=%b I6=%b
        ;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
        $display("Y0=%b Y1=%b
        Y2=%b",Y0,Y1,Y2);

        I0=0;I1=1;I2=0;I3=0;I4=0;I5=0;I6=0;I7=0;
        #1
        $display("I0=%b I1=%b I2=%b I3=%b
        I4=%b I5=%b I6=%b
        ;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
        $display("Y0=%b Y1=%b
        Y2=%b",Y0,Y1,Y2);

        I0=0;I1=0;I2=1;I3=0;I4=0;I5=0;I6=0;I7=0;
        #1
        $display("I0=%b I1=%b I2=%b I3=%b
        I4=%b I5=%b I6=%b
        ;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
        $display("Y0=%b Y1=%b
        Y2=%b",Y0,Y1,Y2);

        I0=0;I1=0;I2=0;I3=1;I4=0;I5=0;I6=0;I7=0;
        #1

        $display("I0=%b I1=%b I2=%b I3=%b
        I4=%b I5=%b
        I6=%b;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
```

Design:

```
//21BCP291
module
Encoder(A0,A1,A2,A3,A4,A5,A6,A7,B0,B1,B2);
input A0,A1,A2,A3,A4,A5,A6,A7;
    output B0,B1,B2;
    assign B0 = A1 | A3 | A5 | A7;
    assign B1 = A2 | A3 | A6 | A7;
    assign B2 = A4 | A5 | A6 | A7;

endmodule
```

```

    $display("I0=%b I1=%b I2=%b I3=%b
I4=%b I5=%b I6=%b
;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
    $display("Y0=%b Y1=%b
Y2=%b",Y0,Y1,Y2);

    I0=0;I1=0;I2=0;I3=0;I4=1;I5=0;I6=0;I7=0;
#1
    $display("I0=%b I1=%b I2=%b I3=%b
I4=%b I5=%b I6=%b
;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
    $display("Y0=%b Y1=%b
Y2=%b",Y0,Y1,Y2);

    I0=0;I1=0;I2=0;I3=0;I4=0;I5=1;I6=0;I7=0;
#1
    $display("I0=%b I1=%b I2=%b I3=%b
I4=%b I5=%b I6=%b
;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
    $display("Y0=%b Y1=%b
Y2=%b",Y0,Y1,Y2);

    I0=0;I1=0;I2=0;I3=0;I4=0;I5=0;I6=1;I7=0;
#1
    $display("I0=%b I1=%b I2=%b I3=%b
I4=%b I5=%b I6=%b
;I7=%b",I0,I1,I2,I3,I4,I5,I6,I7);
    $display("Y0=%b Y1=%b
Y2=%b",Y0,Y1,Y2);
end
    initial
    begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
end
endmodule

```


Output:

```
[2022-10-04 13:26:33 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
I0=1 I1=0 I2=0 I3=0 I4=0 I5=0 I6=0 ;I7=0
Y0=0 Y1=0 Y2=0
I0=0 I1=1 I2=0 I3=0 I4=0 I5=0 I6=0 ;I7=0
Y0=1 Y1=0 Y2=0
I0=0 I1=0 I2=1 I3=0 I4=0 I5=0 I6=0 ;I7=0
Y0=0 Y1=1 Y2=0
I0=0 I1=0 I2=0 I3=1 I4=0 I5=0 I6=0 ;I7=0
Y0=1 Y1=1 Y2=0
I0=0 I1=0 I2=0 I3=0 I4=1 I5=0 I6=0 ;I7=0
Y0=0 Y1=0 Y2=1
I0=0 I1=0 I2=0 I3=0 I4=0 I5=1 I6=0 ;I7=0
Y0=1 Y1=0 Y2=1
I0=0 I1=0 I2=0 I3=0 I4=0 I5=0 I6=1 ;I7=0
Y0=0 Y1=1 Y2=1
I0=0 I1=0 I2=0 I3=0 I4=0 I5=0 I6=0 ;I7=1
Y0=1 Y1=1 Y2=1
Finding VCD file...
./dump.vcd
[2022-10-04 13:26:33 EDT] Opening EPWave...
Done
```

Figure 11: Output of 8:3 Encoder

Waveform:

 


Figure 12: Waveform of 8:3 Encoder

Circuit diagram:

