


Name - Akshat Shah

Roll No - 21BCP322

Sem – III

Digital Electronics and Computer Organization Lab

Course Code – 20CP203P

 

Department of Computer Science Engineering  
School of Technology,  
Pandit Deendayal Energy University

**Date:12-10-2022**

## **Assignment-7**

### **List of Questions:**

**Question 1:** Write a Verilog code to implement BCD to seven segment display Decoder. Prepare the Truth Table and circuits and verify the same using Test Bench.

#### **About Seven segment display:**

- A seven-segment display (SSD) is a form of electronic display device for displaying decimal numbers.
- It has seven segments and we can use it to display  $2^7=128$  character combinations and we can form combinations of display numerical from 0 to 9.
- Each display unit is represented by a dot point.

 


Fig-1: Display of decimal nos using SSD

#### **Applications:**

1. Digital clocks
2. Clock radios
3. Calculators
4. Vehicle odometers

## Test bench:

```
2 //Akshat Shah
3 //21BCP322
4 module tb_segment7;
5
6     reg [3:0] bcd;
7     wire [6:0] seg;
8     integer i;
9
10    // Instantiate the Unit Under Test (UUT)
11    segment7 uut (
12        .bcd(bcd),
13        .seg(seg)
14    );
15
16    //Apply inputs
17    initial begin
18        for(i = 0; i < 10; i = i+1) //run loop for 0 to 15.
19            begin
20                bcd = i;
21                #10; //wait for 10 ns
22                $display("%b", seg);
23            end
24        end
25    initial
26    begin
27        $dumpfile("dump.vcd");
28        $dumpvars(1);
29    end
30 endmodule
31
32
33
```

```
3 module segment7(
4     bcd,
5     seg
6 );
7
8     //Declare inputs, outputs and internal variables.
9     input [3:0] bcd;
10    output [6:0] seg;
11    reg [6:0] seg;
12
13    //always block for converting bcd digit into 7 segment format
14    always @(bcd)
15    begin
16        case (bcd) //case statement
17            0 : seg = 7'b0000001;
18            1 : seg = 7'b1001111;
19            2 : seg = 7'b0010010;
20            3 : seg = 7'b0000110;
21            4 : seg = 7'b1001100;
22            5 : seg = 7'b0100100;
23            6 : seg = 7'b0100000;
24            7 : seg = 7'b0001111;
25            8 : seg = 7'b0000000;
26            9 : seg = 7'b0000100;
27            //switch off 7 segment character when the bcd
28            digit is not a decimal number.
29            default : seg = 7'b1111111;
30        endcase
31    end
32 endmodule
33
```

Fig-1.1 Verilog Code for SSD

## Output:


```
[2022-10-10 02:31:03 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
```

```
VCD info: dumpfile dump.vcd opened for output.
```

```
0000001
1001111
0010010
0000110
1001100
0100100
0100000
0001111
0000000
0000100
```

```
Done
```

Circuit diagram:

 


Truth table:

Decimal Digit	Input lines				Output lines							Display pattern
	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1	2
3	0	0	1	1	1	1	1	1	0	0	1	3
4	0	1	0	0	0	1	1	0	0	1	1	4
5	0	1	0	1	1	0	1	1	0	1	1	5
6	0	1	1	0	1	0	1	1	1	1	1	6
7	0	1	1	1	1	1	1	0	0	0	0	7
8	1	0	0	0	1	1	1	1	1	1	1	8
9	1	0	0	1	1	1	1	1	0	1	1	9

2. Design a 3:8 Decoder using Logisim.

Circuit Diagram:

 


Truth table:

S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

### 3. Design a 3:8 Decoder using two 2:4 Decoder using Logisim.

Circuit diagram:

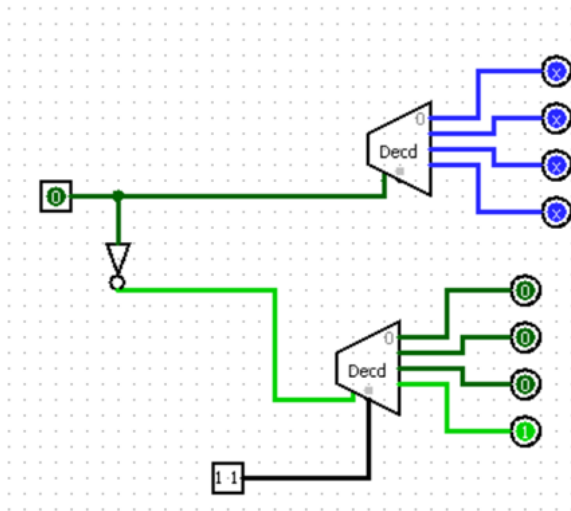

Truth table:

S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

232 - Logic Design / 0.3

$$Q0 = S2' S1' S0'$$

$$Q1 = S2' S1' S0$$

$$Q2 = S2' S1 S0'$$

$$Q3 = S2' S1 S0$$

$$Q4 = S2 S1' S0'$$


$$Q5 = S2 S1' S0$$

$$Q6 = S2 S1 S0'$$

$$Q7 = S2 S1 S0$$

#### 4.Design an 8:3 Priority Encoder using Logisim

Circuit diagram:

 


Truth table:

[illegible]

## 5. Design a 4:1 Multiplexer using Logisim.

Circuit diagram:

 


Truth table:

Selection Lines		Output
$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$



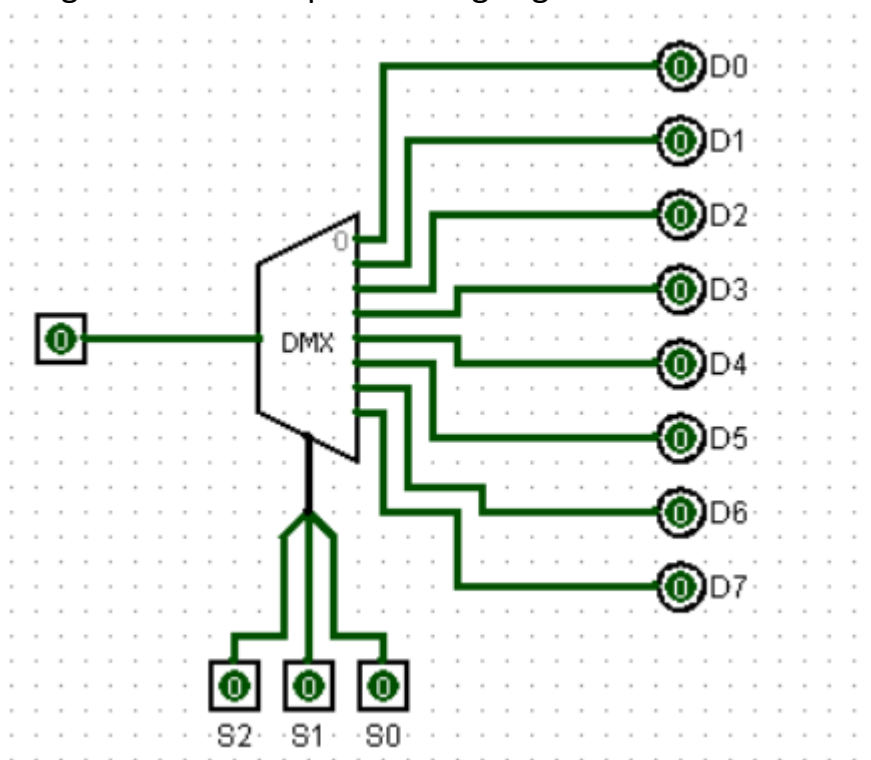6. Design a 1:8 Demultiplexer using Logisim.



Truth table:

INPUT			OUTPUT							
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	d <sub>7</sub>	d <sub>6</sub>	d <sub>5</sub>	d <sub>4</sub>	d <sub>3</sub>	d <sub>2</sub>	d <sub>1</sub>	d <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0