


Name - Akshat Shah

Roll No - 21BCP322

Sem – III

Digital Electronics and Computer Organization Lab

Course Code – 20CP203P

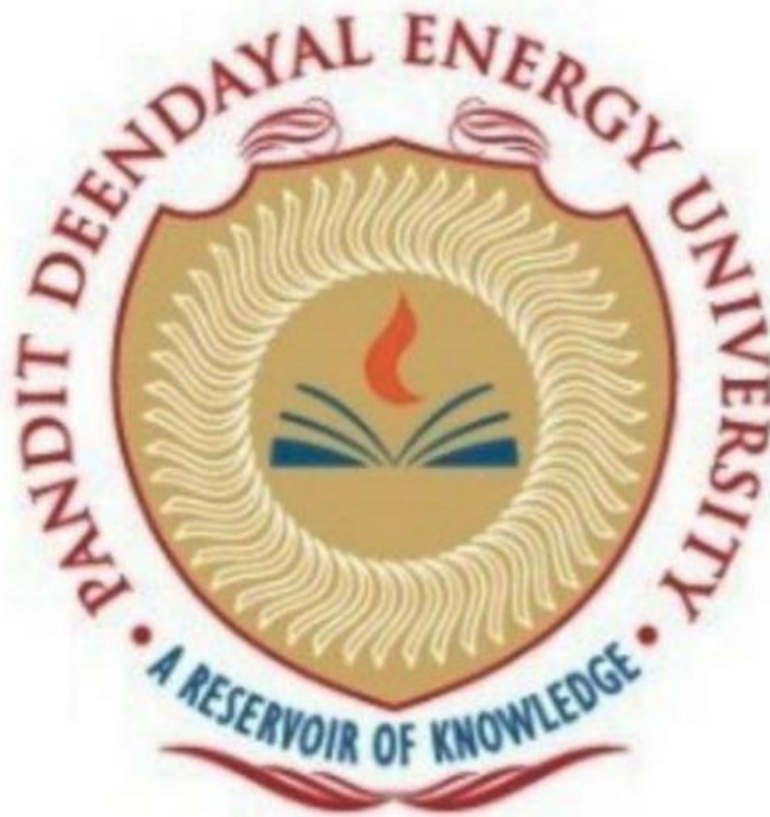

Department of Computer Science Engineering
School of Technology,
Pandit Deendayal Energy University

Date: 07-09-2022

Assignment-4

Aim: To implement Combinational circuits of half adder and full adders

Table of Contents

List of Questions:

Question 1: Write Verilog code for half adder. Test using waveform.

Verilog Code:

Design Code:

```
module HA(input a,b,output carry,sum);  
assign sum=a^b;  
assign carry=a&b;  
endmodule
```

Test bench Code:

```
module tb_HA;  
reg A,B; wire C,S;  
HA a1(A,B,C,S);  
  
initial  
begin  
    A=0;B=0; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",C);  
    $display("s=%b",S); A=0;B=1; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",C);  
    $display("s=%b",S); A=1;B=0; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",C);  
    $display("s=%b",S); A=1;B=1; #1;  
    $display("a=%b and b=%b",A,B);  
  
    $display("c=%b",C);  
    $display("s=%b",S);  
end
```

```

initial begin

$dumpfile("dump.vcd");

$dumpvars(1);

end

endmodule

```

Output:

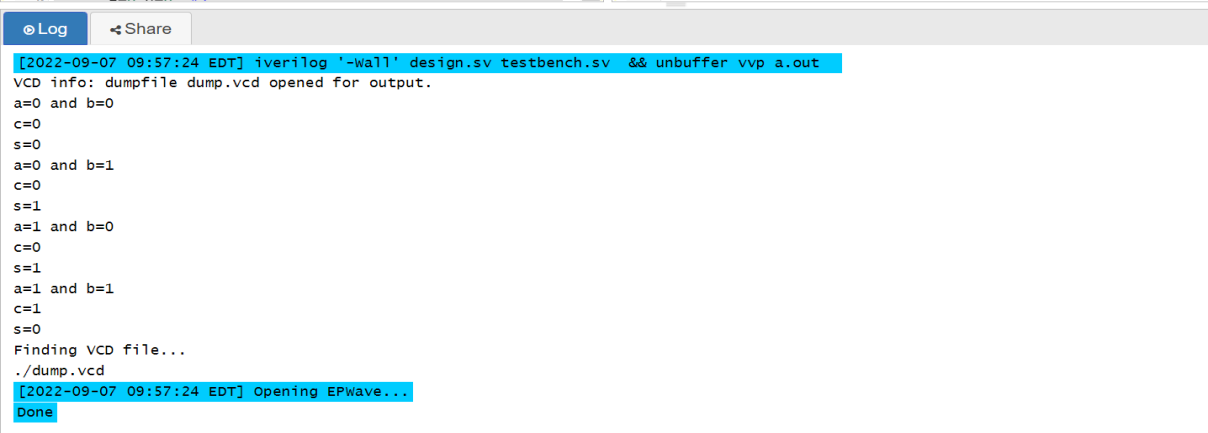


Fig 1.1.2 - Output as Truth table

Waveform:


 


Fig 1.1.3- Waveform for output

Circuit diagram:

 

Question 2. Write Verilog code for full adder. Test using waveform.

Verilog Code:

Design Code:

```
module FA(input a,b,c_in,output sum,c_out);  
assign sum=a^b^c_in;  
assign c_out=((a^b)&c_in)|(a&b);  
endmodule
```

Test bench code:

```
module tb_FA;  
reg A,B,C; wire S,Co;  
FA f1(A,B,C,S,Co);  
initial begin  
A=0;B=0;C=0;#1;  
$display("A=%b and B=%b and C=%b",A,B,C);  
$display("s=%b",S);  
$display("carry=%b",Co);  
  
A=0;B=1;C=0;#1;  
$display("A=%b and B=%b and C=%b",A,B,C);  
$display("s=%b",S);  
$display("carry=%b",Co);  
  
A=0;B=1;C=1;#1;  
$display("A=%b and B=%b and C=%b",A,B,C);  
$display("s=%b",S);  
$display("carry=%b",Co);  
  
A=1;B=0;C=0;#1;  
$display("A=%b and B=%b and C=%b",A,B,C);  
$display("s=%b",S);  
$display("carry=%b",Co);  
  
A=1;B=0;C=1;#1;  
$display("A=%b and B=%b and C=%b",A,B,C);  
$display("s=%b",S);  
$display("carry=%b",Co);
```

```

A=1;B=1;C=0;#1;
$display("A=%b and B=%b and C=%b",A,B,C);
$display("s=%b",S);
$display("carry=%b",Co);

```

```

A=1;B=1;C=1;#1;
$display("A=%b and B=%b and C=%b",A,B,C);
$display("s=%b",S);
$display("carry=%b",Co);

```

end

initial begin

```
$dumpfile("dump.vcd");
```

```
$dumpvars(1);
```

End

endmodule

Output:

```

[2022-09-07 10:00:16 EDT] iverilog '-Wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
A=0 and B=0 and C=0
s=0
carry=0
A=0 and B=0 and C=1
s=1
carry=0
A=0 and B=1 and C=0
s=1
carry=0
A=0 and B=1 and C=1
s=0
carry=1
A=1 and B=0 and C=0
s=1
carry=0
A=1 and B=0 and C=1
s=0
carry=1
A=1 and B=1 and C=0
s=0
carry=1
A=1 and B=1 and C=1
s=1
carry=1
Finding VCD file...
/dump.vcd

```


Fig 1.2.2 - Output as truth table

Waveform:



Fig 1.2.3- Waveform of output

Circuit diagram:

 

Question 4. Write Verilog code for full adder using module instantiation of half adder.
Test using waveform.

Verilog Code:

Design Code:

```
module HA(input a,b,output s,c);  
    assign s=a^b;  
    assign c=a&b; endmodule  
  
module FA(input p,q,r,output sum,carry); wire s1,c1,c2;  
    HA h1(p,q,s1,c1);  
    HA h2(s1,r,sum,c2);  
    or(carry,c1,c2);  
endmodule
```

Test bench Code:

```
module tb_FA;  
    reg A,B,C; wire SUM,CARRY;  
    FA f1(A,B,C,SUM,CARRY);  
    initial begin  
        A=0;B=0;C=0;#1;  
        $display("A=%b and B=%b and C=%b",A,B,C);  
        $display("s=%b",SUM);  
        $display("carry=%b",CARRY);  
  
        A=0;B=0;C=1;#1;  
        $display("A=%b and B=%b and C=%b",A,B,C);  
        $display("s=%b",SUM);  
        $display("carry=%b",CARRY);  
  
        A=0;B=1;C=0;#1  
        $display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY);
```

```
A=0;B=1;C=1;#1;
```

```
$display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY);
```

```
A=1;B=0;C=0;#1;
```

```
$display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY);
```

```
A=1;B=0;C=1;#1;
```

```
$display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY);
```

```
A=1;B=1;C=0;#1;
```

```
$display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY);
```

```
A=1;B=1;C=1;#1;
```

```
$display("A=%b and B=%b and C=%b",A,B,C);
```

```
$display("s=%b",SUM);
```

```
$display("carry=%b",CARRY); end
```

```
initial begin
```

```
$dumpfile("dump.vcd");
```

```
$dumpvars(1); end  
  
endmodule
```

Output:

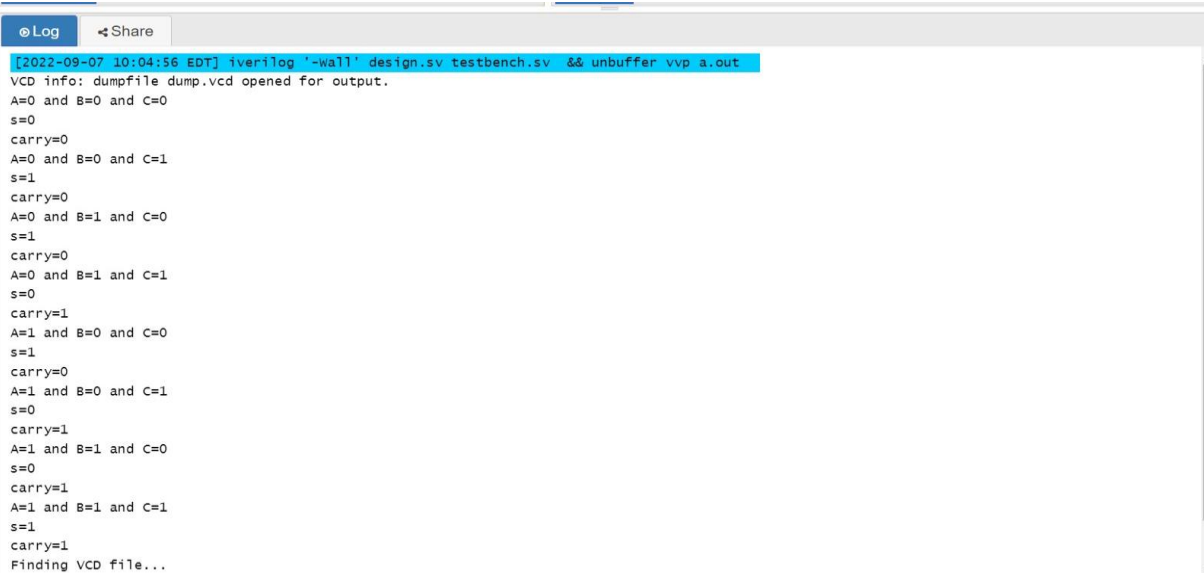


Fig 1.3.2 - Output as truth table

Waveform:

 


Fig 1.3.3- Waveform of full adder

Question 5. Write Verilog code for half adder using only NAND gate. Test using waveform.

Verilog Code:

Design Code:

```
module HA(input a,b,output sum,carry);  
wire a_not,b_not,x,y;  
nand(a_not,a); nand(b_not,b);  
nand(x,a_not,b);  
nand(y,a,b_not);  
nand(sum,x,y);  
nand(carry,z);    // Calculating Carry  
endmodule
```

Testbench Code:

```
module tb_FA; reg A,B;  
wire SUM,CARRY;  
HA f1(A,B,SUM,CARRY);  
initial begin  
    A=0;B=0; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",CARRY);  
    $display("s=%b",SUM); A=0;B=1; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",CARRY);  
    $display("s=%b",SUM); A=1;B=0; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",CARRY);  
    $display("s=%b",SUM);  
    A=1;B=1; #1;  
    $display("a=%b and b=%b",A,B);  
    $display("c=%b",CARRY);  
    $display("s=%b",SUM);  
end
```

```

end

initial begin

$dumpfile("dump.vcd");

$dumpvars(1); end

endmodule

```

Output:

```

[2022-09-07 10:10:19 EDT] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
design.sv:10: warning: implicit definition of wire logic tb_FA.f1.z.
VCD info: dumpfile dump.vcd opened for output.
a=0 and b=0
c=0
s=0
a=0 and b=1
c=0
s=1
a=1 and b=0
c=0
s=1
a=1 and b=1
c=1
s=0
Finding VCD file...
./dump.vcd
[2022-09-07 10:10:19 EDT] Opening EPWave...
Done

```

Fig 1.4.2- output as truth table

Waveform:


 


Fig 1.4.3- Waveform of output

Circuit diagram:

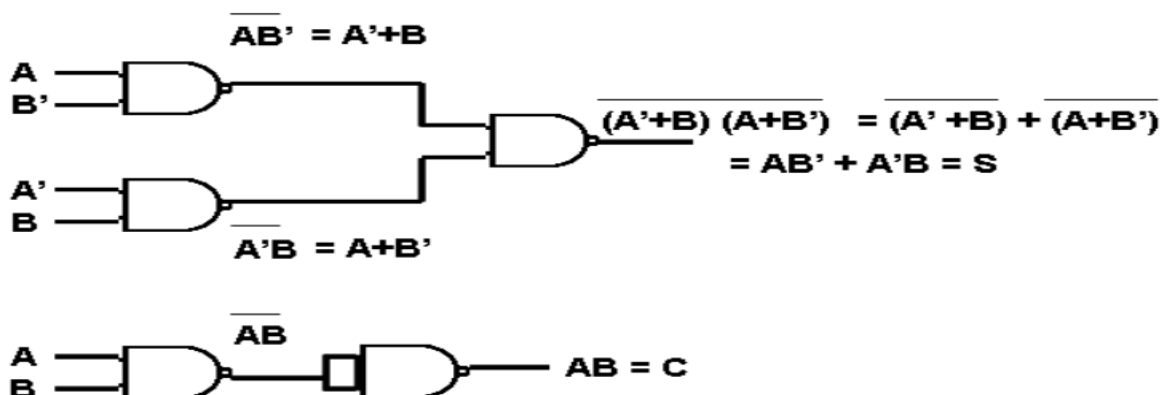

Question 6. Write Verilog code for half adder using only NOR gate. Test using waveform.

Verilog Code:

Design Code:

```
module HA(input a,b,output sum,carry);
wire a_not,b_not,x,y,w;

    nor(a_not,a);
    nor(b_not,b);
    nor(x,a,b_not);
    nor(y,a_not,b);
    nor(w,x,y);
    nor(sum,w);
    nor(carry,a_not,b_not);

endmodule
```

Test bench Code:

```
module tb_FA;

    reg A,B;
    wire SUM,CARRY;
    HA f1(A,B,SUM,CARRY);

    initial
    begin
        A=0;B=0; #1;
        $display("a=%b and b=%b",A,B);
        $display("c=%b",CARRY);
        $display("s=%b",SUM);

        A=0;B=1; #1;
        $display("a=%b and b=%b",A,B);
        $display("c=%b",CARRY);
        $display("s=%b",SUM);
    end
endmodule
```

```

A=1;B=0; #1;

$display("a=%b and b=%b",A,B);

$display("c=%b",CARRY);

$display("s=%b",SUM);

A=1;B=1; #1;

$display("a=%b and b=%b",A,B);

$display("c=%b",CARRY);

$display("s=%b",SUM); end

initial begin

    $dumpfile("dump.vcd");

    $dumpvars(1); end

endmodule

```

Output:

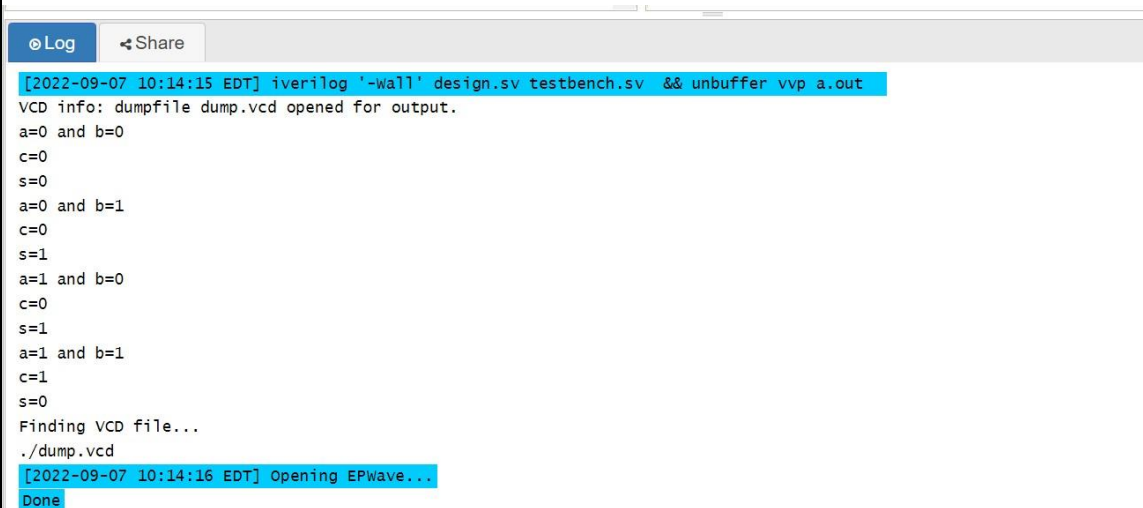


Fig 1.5.2- Output as truth table

Waveform:


 


Fig 1.5.3- Waveform of output

Circuit diagram:

 

Half adder using NOR gates