

Name - Akshat Shah


Roll No - 21BCP322

Sem – III

Digital Electronics and Computer Organization
Lab

Course Code – 20CP203P

Department of CSE

 

Assignment-1

EXERCISE 1: Design the following logic functions using basic gates and test the output using truth table.

1.1: $Y = ABC + DE + F$

CIRCUIT DIAGRAM:

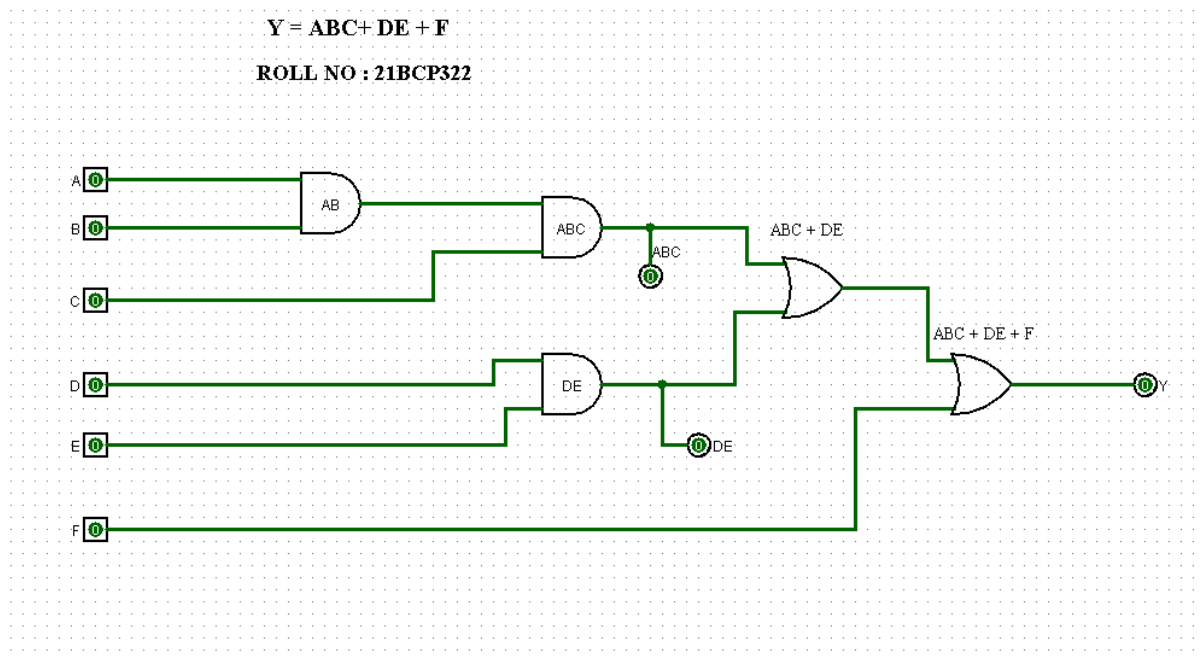


Figure 1.1 Digital Circuit representing $Y = ABC + DE + F$

Truth table:

A	B	C	D	E	F	ABC	Y	DE
0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	0	1	0
0	0	0	0	1	0	0	0	0
0	0	0	0	1	1	0	1	0
0	0	0	1	0	0	0	0	0

[illegible]

1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	0
1	1	1	0	0	1	1	1	0
1	1	1	0	1	0	1	1	0
1	1	1	0	1	1	1	1	0
1	1	1	1	0	0	1	1	0
1	1	1	1	0	1	1	1	0
1	1	1	1	1	0	1	1	1
1	1	1	1	1	1	1	1	1

Table 1.1 Representing Truth table of $Y = ABC + DE + F$

1.2: $Z = A'B' + AB' + A'B + AB$

CIRCUIT DIAGRAM -:

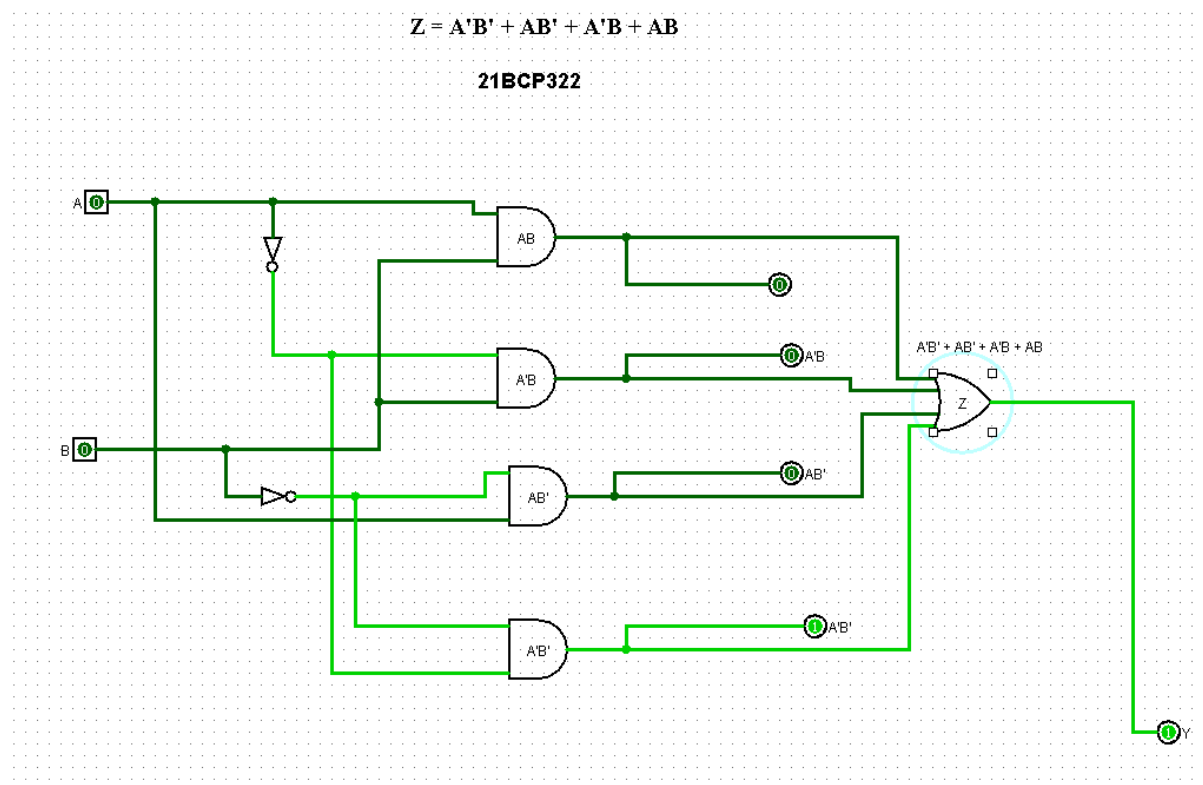


Figure 1.2 Representing Circuit of $Z = A'B' + AB' + A'B + AB$

Truth table:

A	B	AB	AB'	A'B	A'B'	Y
0	0	0	0	0	1	1
0	1	0	1	0	0	1
1	0	0	0	1	0	1
1	1	1	0	0	0	1

Table 1.2 Representing truth table of $Z = A'B' + AB' + A'B + AB$

$$1.3: K = (A'+B')(A+B')(A'+B)(A+B)$$

CIRCUIT DIAGRAM:

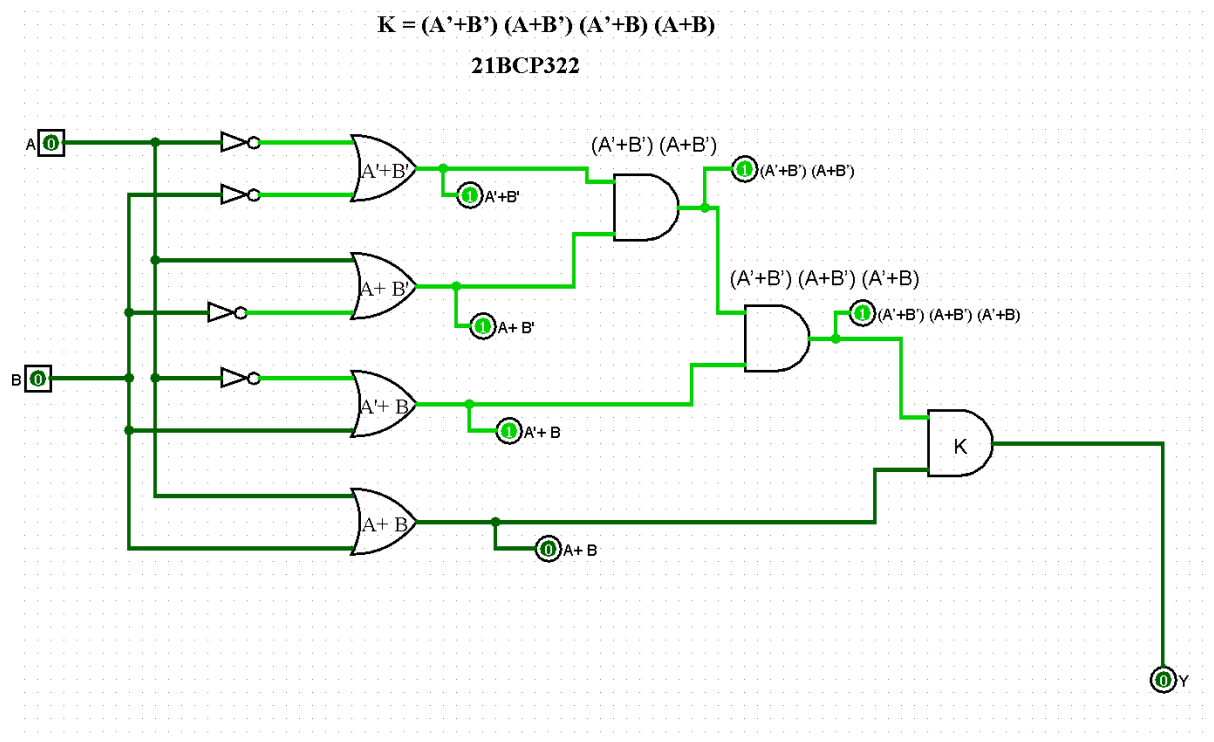


Figure 1.3 Representing Circuit of $K = (A'+B')(A+B')(A'+B)(A+B)$

Truth table:

A	B	ABAB	AB	ABABAB	AB2	AB3	AB4	Y
0	0	1	1	1	1	1	0	0
0	1	0	1	0	0	1	1	0

1	0	1	1	0	1	0	1	0
1	1	0	0	0	1	1	1	0

EXERCISE 2: Design the verify the functionality using existing library of basic gates in Logisim.

2.1: $Y = ((A+B).(C+D+E))'$

CIRCUIT DIAGRAM -:

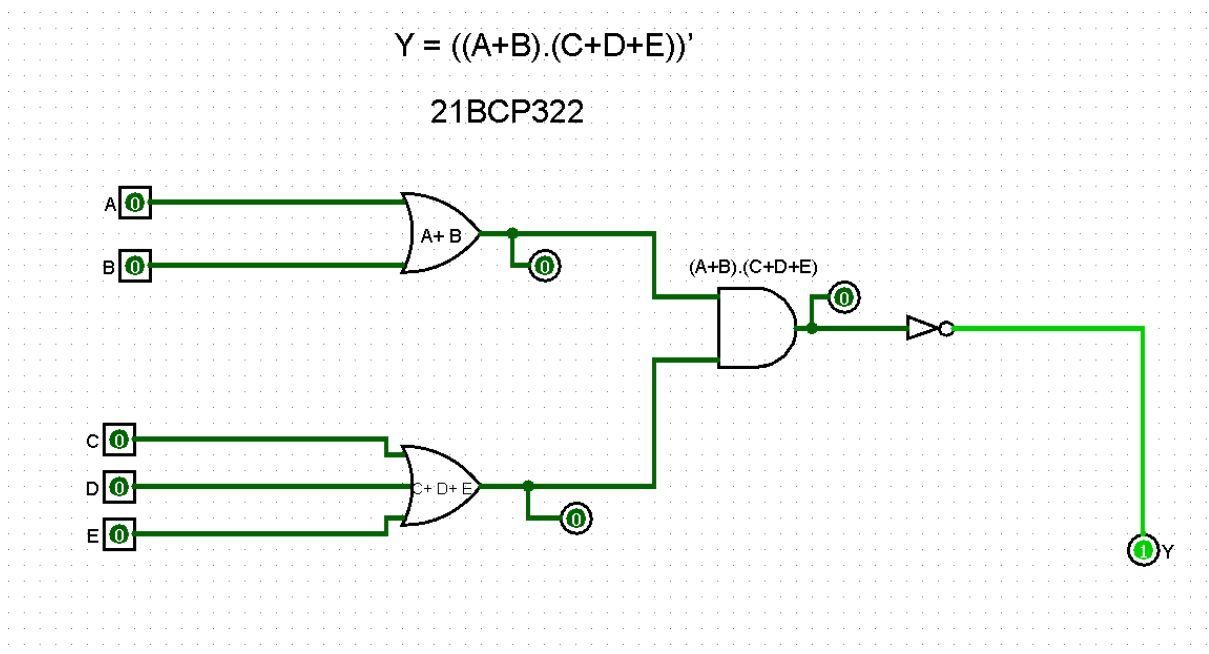


Figure 2.1 Representing Circuit of $Y = ((A+B).(C+D+E))'$

Truth table:

A	B	C	D	E	x	y	z	Y
0	0	0	0	0	0	0	0	1
0	0	0	0	1	0	0	1	1
0	0	0	1	0	0	0	1	1
0	0	0	1	1	0	0	1	1
0	0	1	0	0	0	0	1	1
0	0	1	0	1	0	0	1	1
0	0	1	1	0	0	0	1	1
0	0	1	1	1	0	0	1	1
0	1	0	0	0	1	0	0	1

0	1	0	0	1	1	1	1	0
0	1	0	1	0	1	1	1	0
0	1	0	1	1	1	1	1	0
0	1	1	0	0	1	1	1	0
0	1	1	0	1	1	1	1	0
0	1	1	1	0	1	1	1	0
0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	0	0	1
1	0	0	0	1	1	1	1	0
1	0	0	1	0	1	1	1	0
1	0	0	1	1	1	1	1	0
1	0	1	0	0	1	1	1	0
1	0	1	0	1	1	1	1	0
1	0	1	1	0	1	1	1	0
1	0	1	1	1	1	1	1	0
1	1	0	0	0	1	0	0	1
1	1	0	0	1	1	1	1	0
1	1	0	1	0	1	1	1	0
1	1	0	1	1	1	1	1	0
1	1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1	0
1	1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0
1	1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0

Table 2.1 Represents truth table of $Y = ((A+B).(C+D+E))'$

2.2 $F = ((A.B')' + (A'B'))'$

Circuit diagram:

$$F = ((A.B')' + (A'B')')'$$

21BCP322

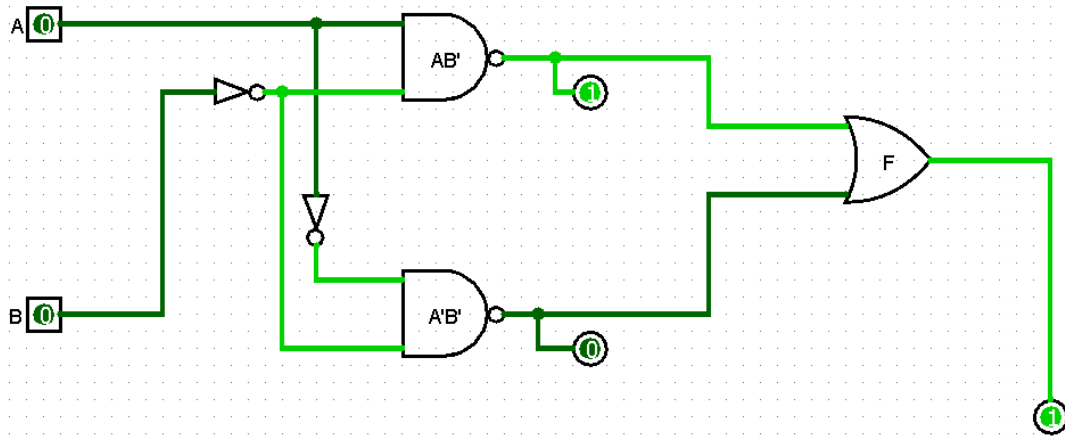


Figure 2.2 Representing Circuit of $F = ((A.B')' + (A'B')')'$

Truth table:

A	B	x	y	z
0	0	1	0	0
0	1	1	1	0
1	0	0	1	0
1	1	1	1	0

Table 2.2 represents truth table of $F = ((A.B')' + (A'B')')'$

2.3: $K = ((A' + B)'.(A' + B'))'$

Circuit Diagram:

$$K = ((A'+B)'.(A'+B')')'$$

21BCP322

 


Figure 2.3 Representing Circuit of $K = ((A'+B)'.(A'+B')')'$

Truth table:

A	B	x	y	z
0	0	0	0	1
0	1	0	0	1
1	0	1	0	1
1	1	0	1	1

Table 2.3 represents truth table of $K = ((A'+B)'.(A'+B')')'$

EXERCISE 3 -: For each of the following problem statement, design a circuit, describe a Truth table and verify the outcome using Logisim.

3.1 -: Implement the functionality of XOR gate using only NAND gates.

Circuit Diagram:

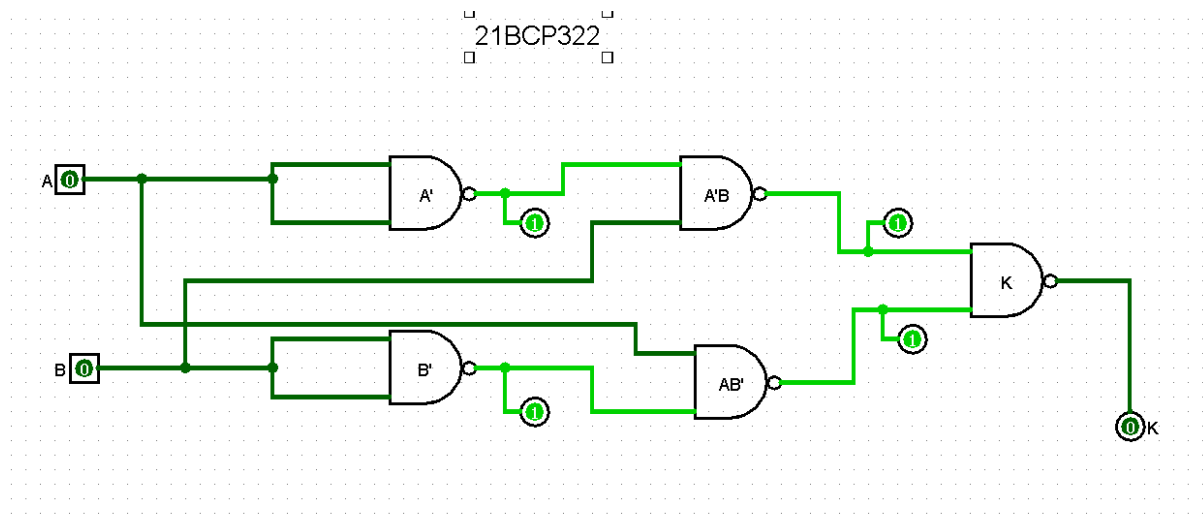


Figure 3.1 Representing Circuit of XOR gate using NAND gates

Truth table:

A	B	x	y	z	u	K
0	0	1	1	1	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	1	1	0	0

3.2: Implement the functionality of XNOR gate using only NOR gates.

CIRCUIT DIAGRAM:

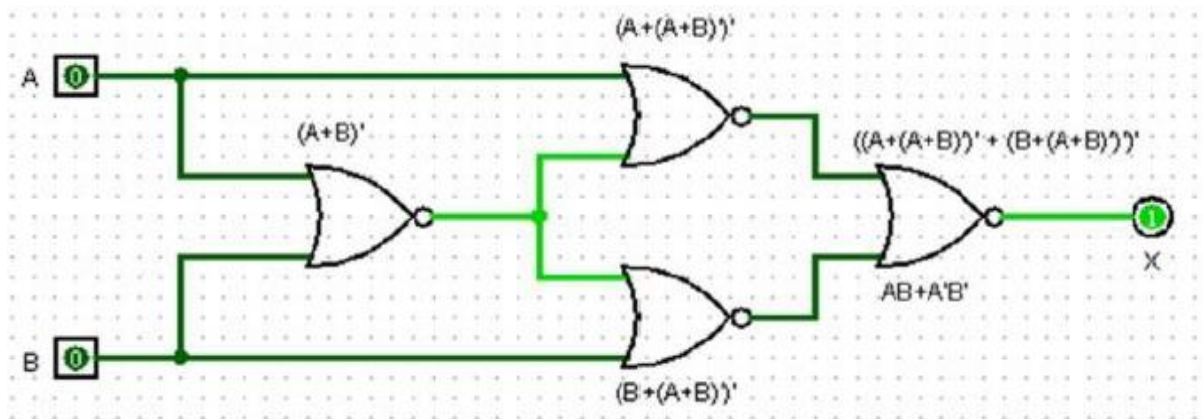


Figure 3.2 Representing Circuit of XNOR gate using NOR gates

Truth Table:

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

Table 3.2 represents the truth table of XNOR gate

3.3 -: Implement the functionality of AND gate using only NAND gates.

CIRCUIT DIAGRAM

 


Figure 3.3 Representing Circuit of AND gate using NAND gate

Truth table:

A	B	x	Y
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

Table 3.3 represents truth table of AND gate

3.4: Implement the functionality of OR gate using only NOR gates.

CIRCUIT DIAGRAM:

 


Figure 3.4 Representing Circuit of OR gate using NOR gates

Truth table:

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Table 3.4 represents truth table of OR gate

3.5: Implement the functionality of NOT gate using only NAND gate.

CIRCUIT DIAGRAM:

 


Figure 3.5 Representing Circuit of NOT gate using NAND gate

Truth table:

A	X
0	1
1	0

Table 3.5 represents truth table of NOT gate